

2IC30: Computer Systems Registers, Random-Access Memories and Finite State Automata.

Jan Friso Groote




TU / **e**



Technische Universiteit
Eindhoven
University of Technology

Where innovation starts

 A microprocessor stores data in registers



  Clocked D-Flip-Flop (or: Edge-Triggered FF)





edge-triggered D-flip-flop

- on $C \uparrow$ then $Q := D$ and $Q' := \neg D$: the outputs copy D on every *upgoing transition* on C .

Requirement:

- Input D must be *stable* only during a short interval around $C \uparrow$: the *setup-and-hold interval*.

Clocked D-Flip-Flop with Enable

  

clocked D-flip-flop,
with enable

- **on $C \uparrow$ then $Q := D$ and $Q' := \neg D$:** the outputs copy D on every *upgoing transition* on C , but *only if* $E = 1$. When $E = 0$ transitions on C have no effect.
- **Application:** to build *registers* that must not assume new values on every clock transition.

Building a Register

Register

- Collection of Flip-Flops, with
- common clock and enable signals.

n -bits register:


- Register containing n Flip-Flops.

Application


- Number processing systems, like computers

Example: a 4-bit Register


4-bit clocked register, with enable

 


symbol

 

alternative symbol

 


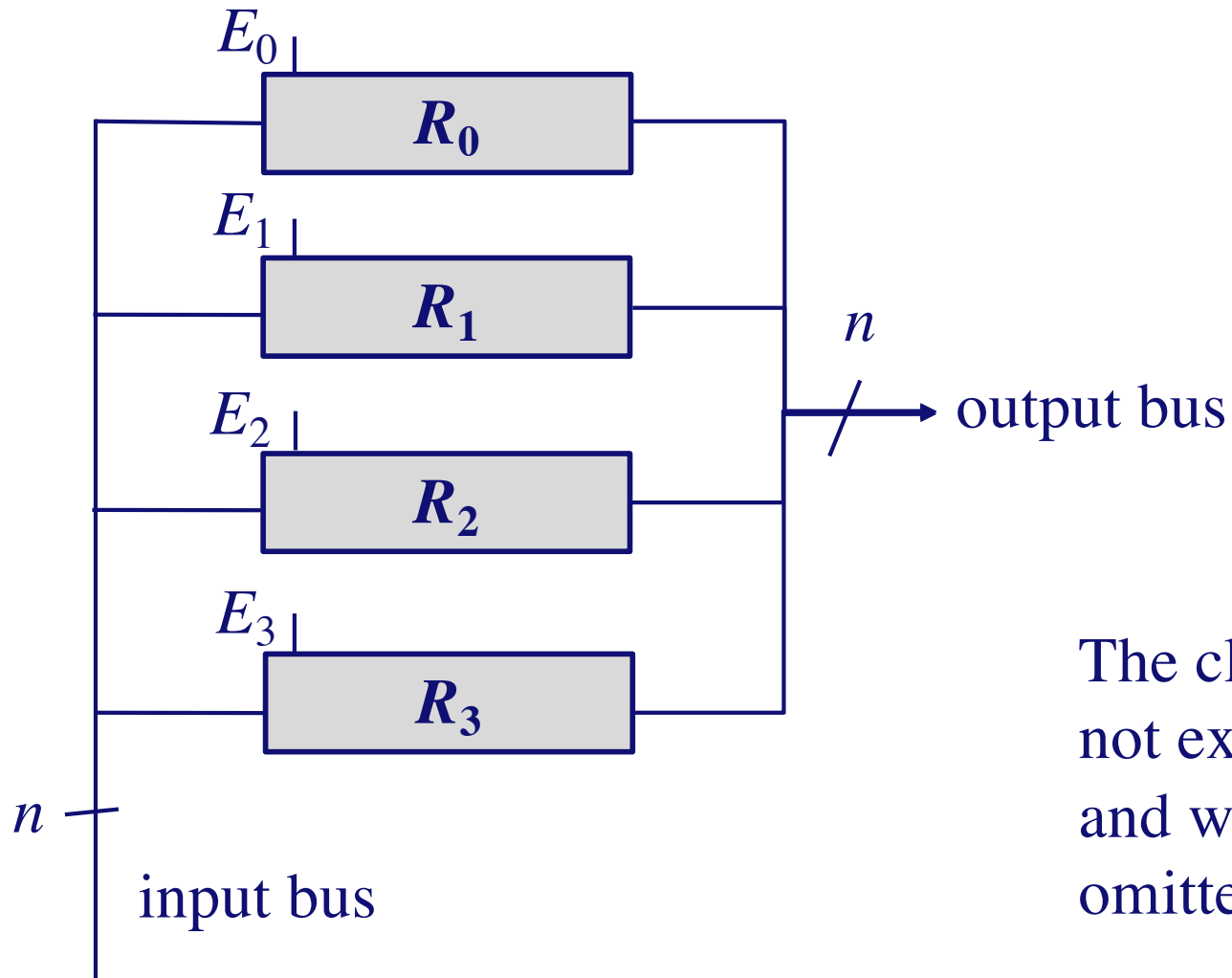n -bit registers connected to the same input and output buses.




The clock signal is not explicitly drawn, and will in general be omitted.

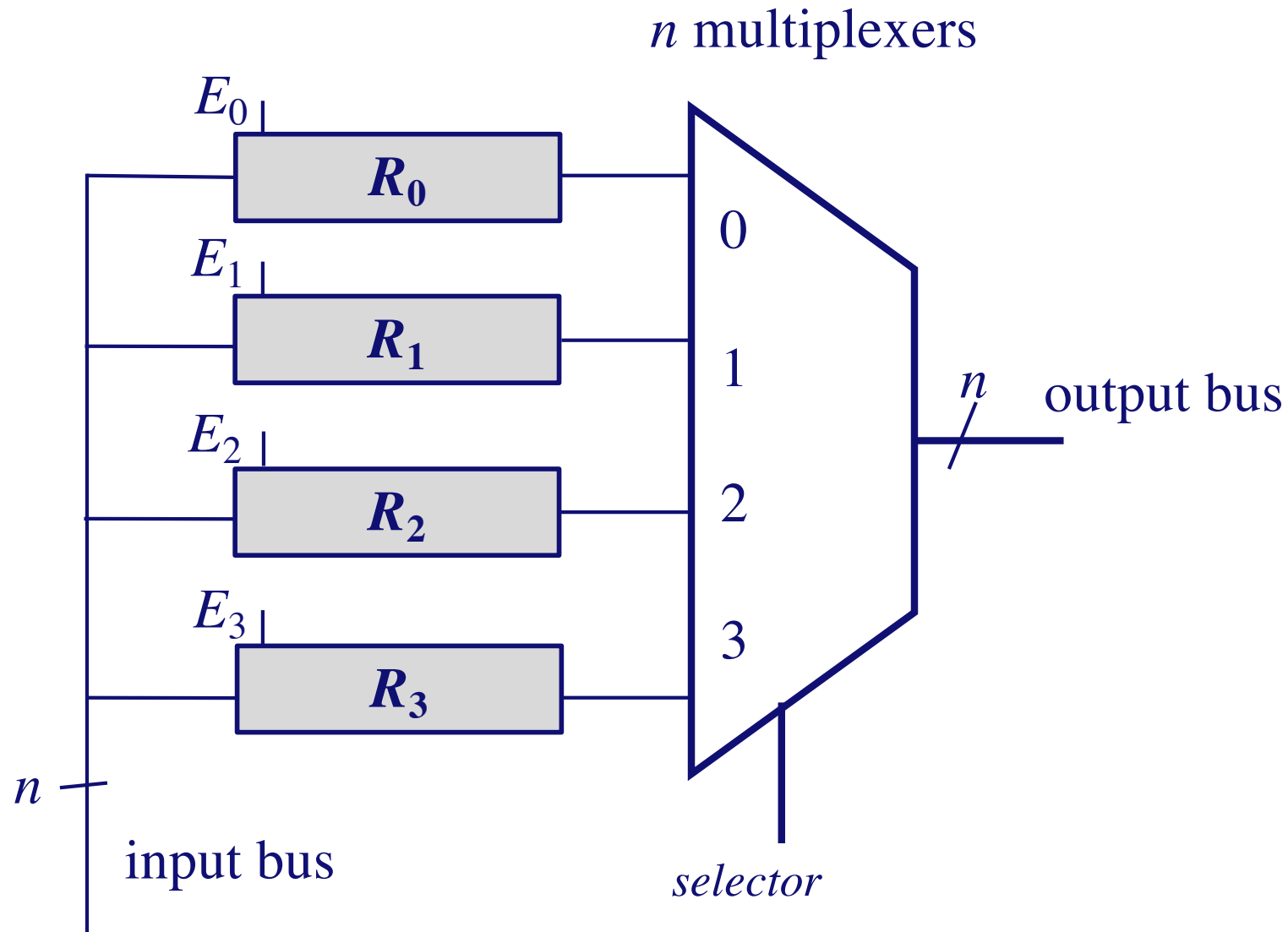
n -bit registers connected to the same input and output buses.



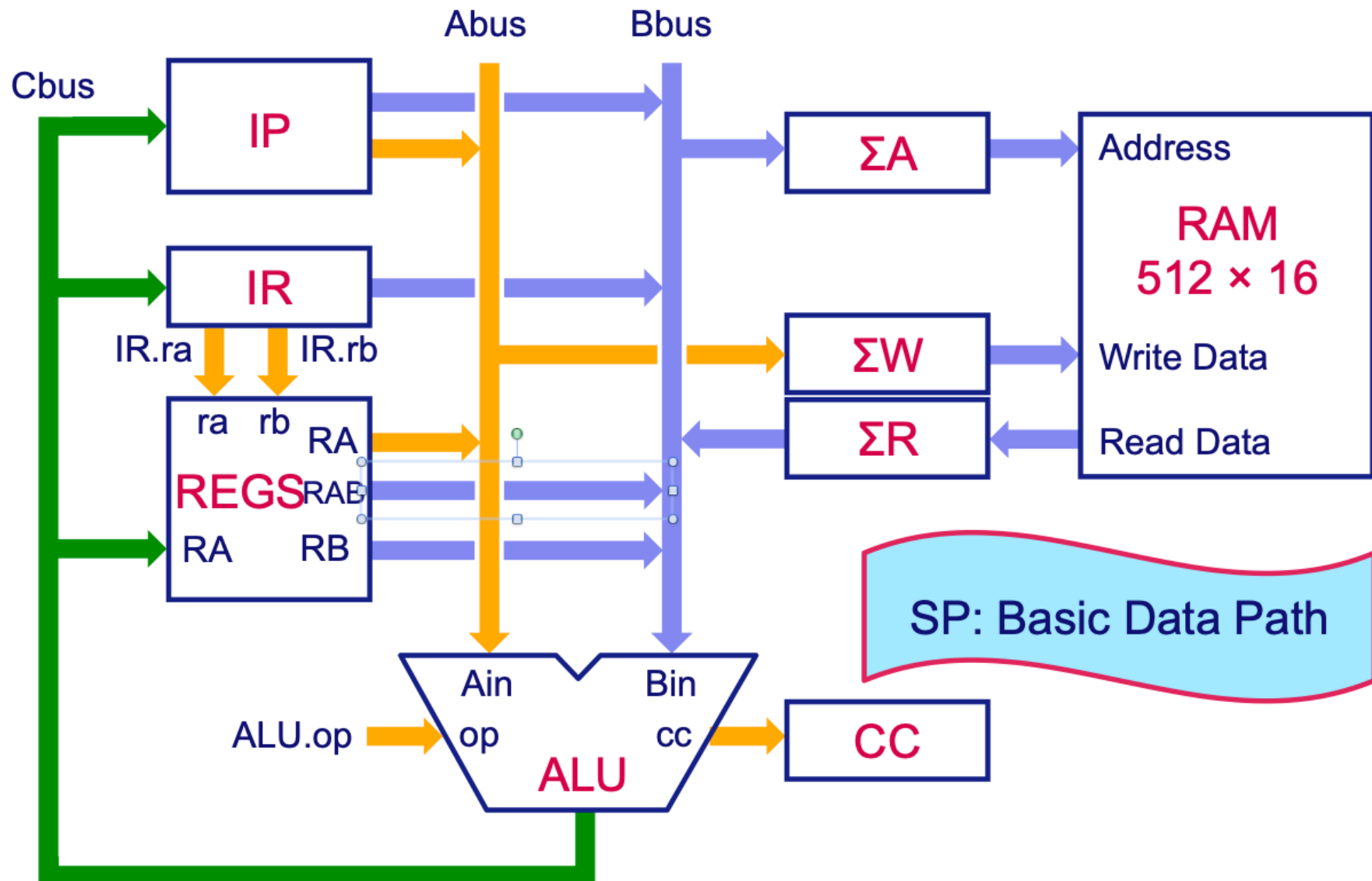A microprocessor stores data in registers




Simple Processor: Data Path

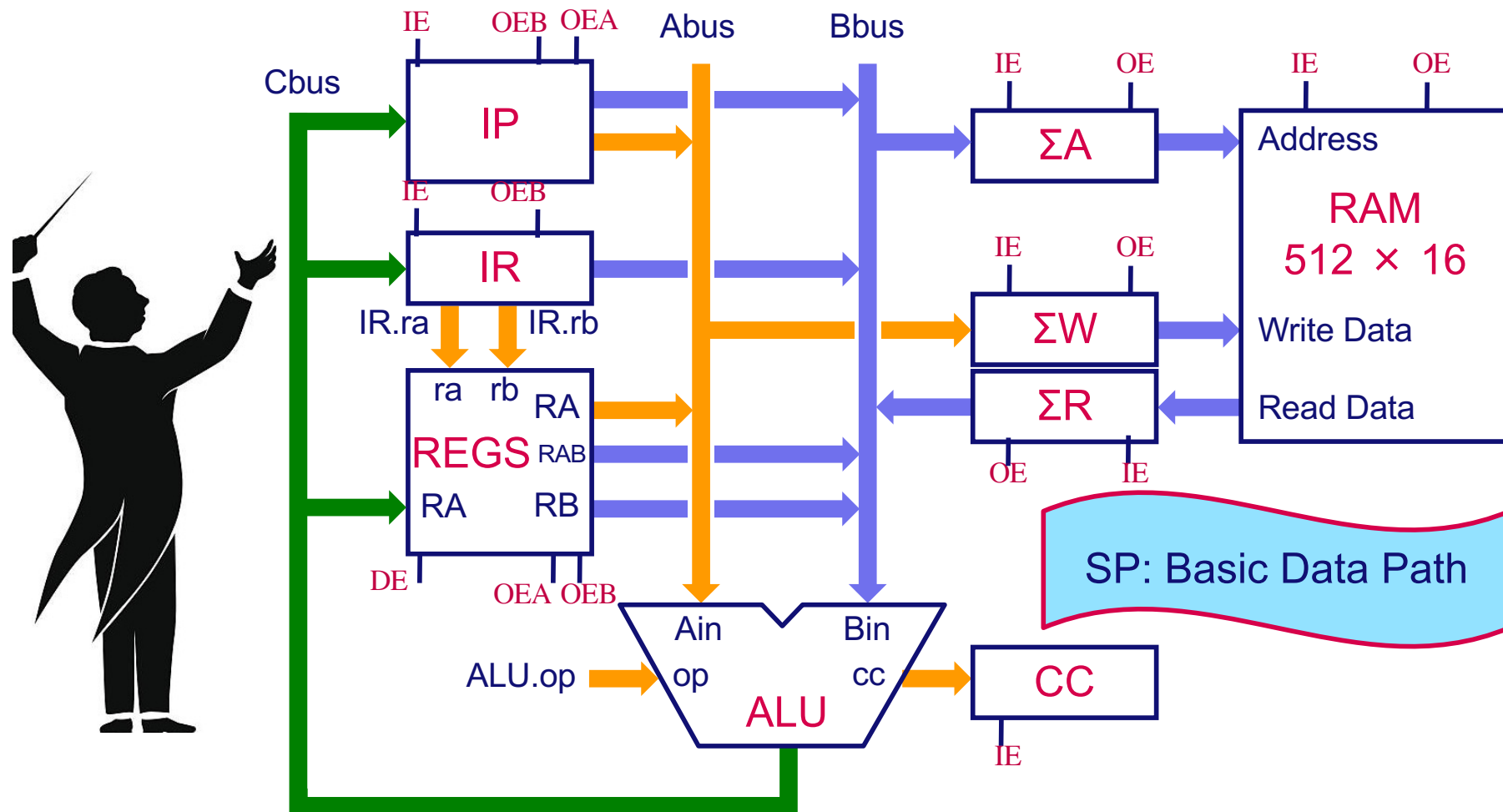

- Abus: IP or RA
- Bbus: IP, IR, ΣR, RB or RAB
- REGS: 2 Reads and 1 Write, simultaneously, ra[1..0] and rb[1..0] select registers

3-State Outputs

 

CMOS output stage...


... behaves like switches

output value “Z” :
not connected, high impedance

| a | b | output |
|---|---|--------------------|
| 0 | 0 | 1 |
| 1 | 0 | Z |
| 1 | 1 | 0 |
| 0 | 1 | 💀 (short circuit!) |

3-State Outputs: Use

symbol

 


truth table

| OE | in | out |
|----|----|-----|
| 0 | 0 | Z |
| 0 | 1 | Z |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

- **Application:** 3-state outputs may be connected together, *provided* at any moment in time *at most one* of the OE-inputs is 1.
- If all OE-inputs are 0: the output equals Z.
- If one OE-input is 1: the output equals the “corresponding” input.
- Thus, cheap and extensible multiplexers can be built.


3-State Outputs: building a 4-input Multiplexer

4-input MUX (symbol)

 


- **problem:** how to connect the OE-signals?
- **solution:** use a *2→4-decoder* !

4-input MUX from 3-state buffers

 

2→4 -decoder


2→4 decoder (symbol)

 

truth table

| E | s_1 | s_0 | d_3 | d_2 | d_1 | d_0 |
|-----|-------|-------|-------|-------|-------|-------|
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 |


2→4 decoder: circuit

 


more general: $n \rightarrow 2^n$ decoder

Application: 4-input Multiplexer, with enable

4-input MUX from 3-state buffers

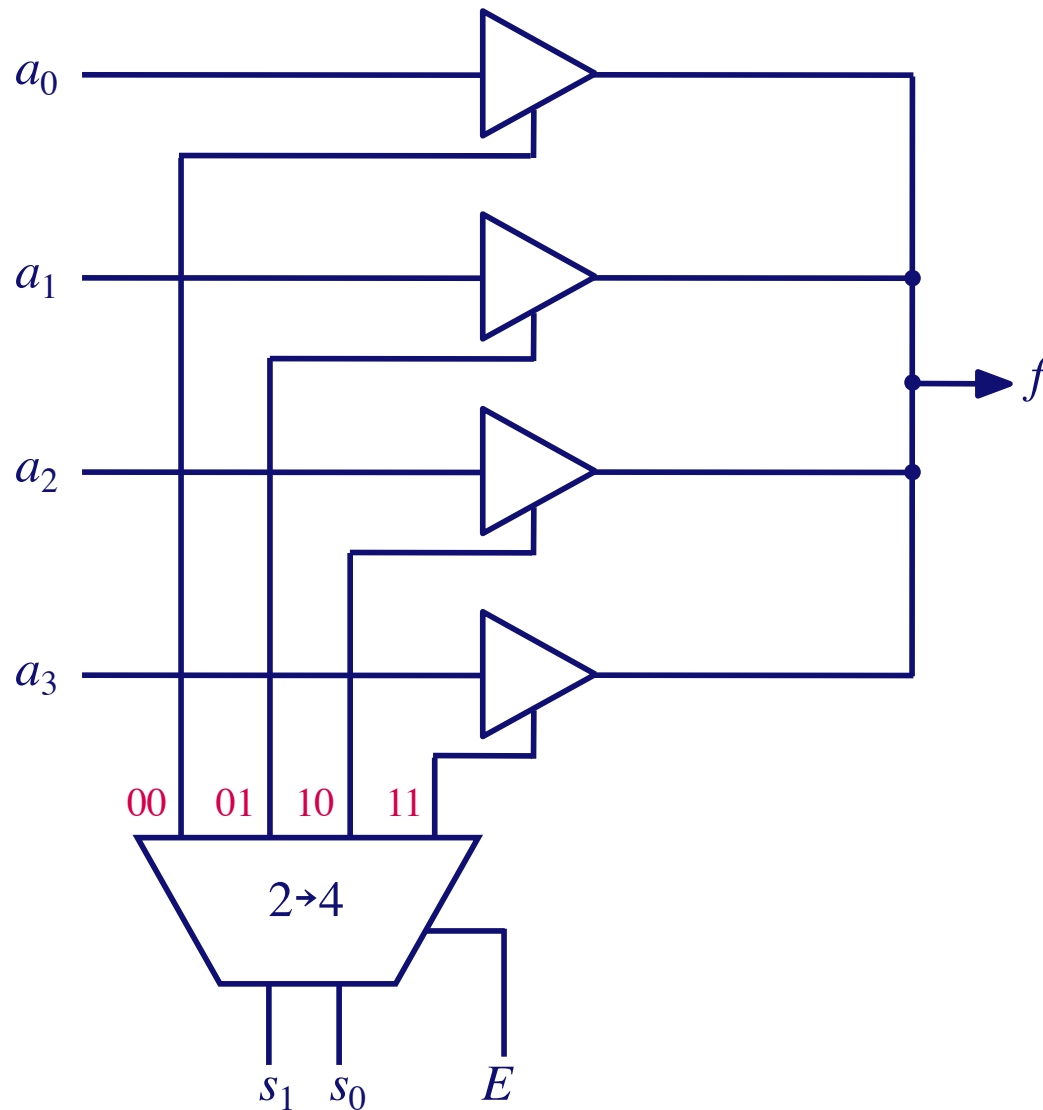


D-Latch with 3-state outputs

 

Property

 
- The *output buffers* are placed *behind* the latch and its internal feedback wiring: the latch can be changed state *even* if the outputs are *disabled*.



D-flip flop with
3-state outputs

RAM: Random-Access Memory

4-bit RAM
with four address.

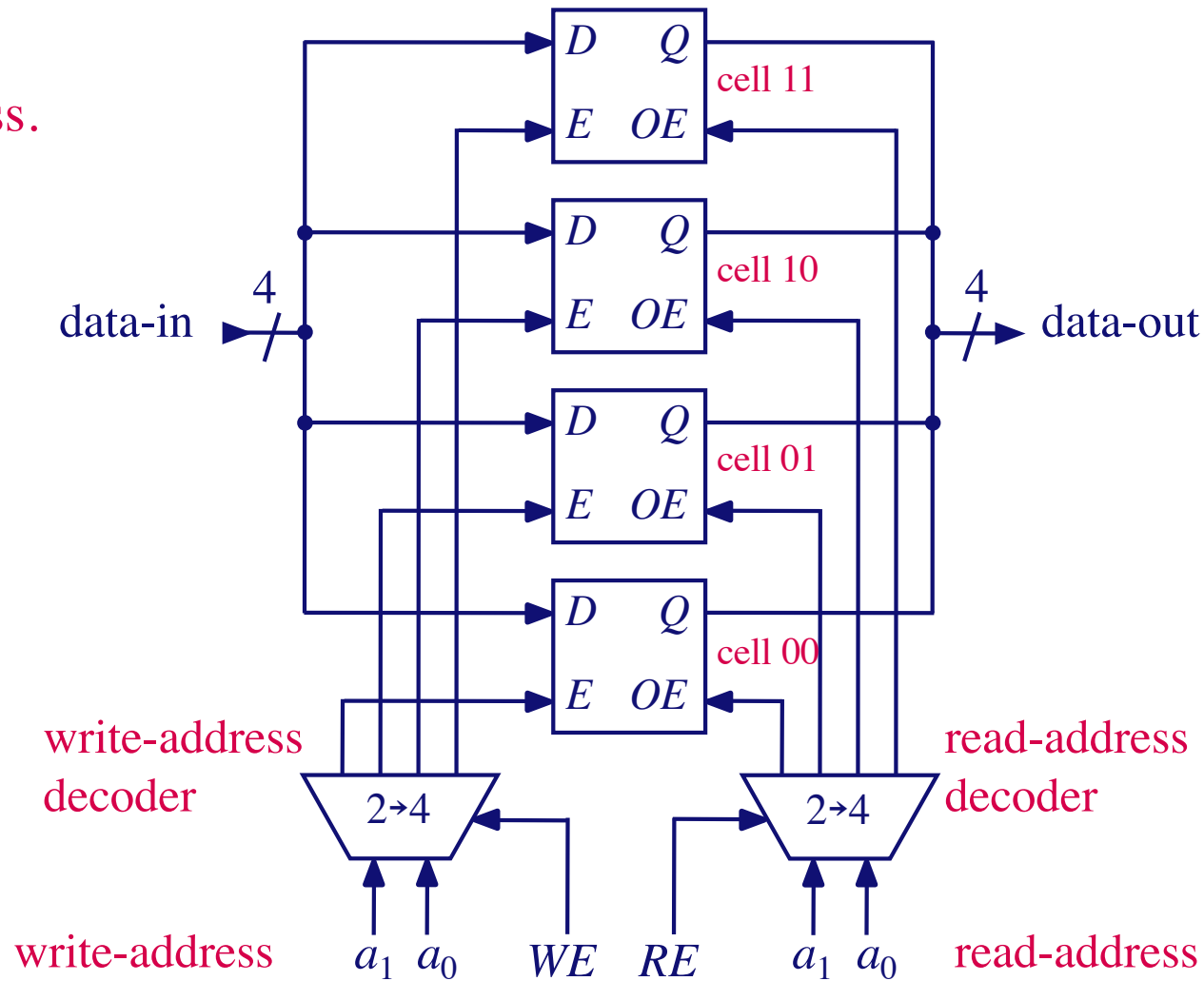


 Questions?



Systems with memory

- ❑ Combinatorial circuits have no memory: output values only depend on on current input values
- ❑ To allow behaviour to depend on (values from) the past, we need different circuits: *sequential circuits*
- ❑ A sequential lock only opens if a series of input values is presented in a very specific order



Behaviour of a system (circuit) is determined by the current input values and (input) values from the past

Finite Automata: the On-Off Switch

Specification

If the push button is pressed, the light goes “on”, and stays “on”; if the same button is pressed again the light goes “off”, and stays “off”, and so on indefinitely.

a incoming arrow identifies the “initial state”


Variables

$\neg p$: the push button is “open”

p : the push button is “closed”

$\neg x$: the light is “off”

x : the light is “on”

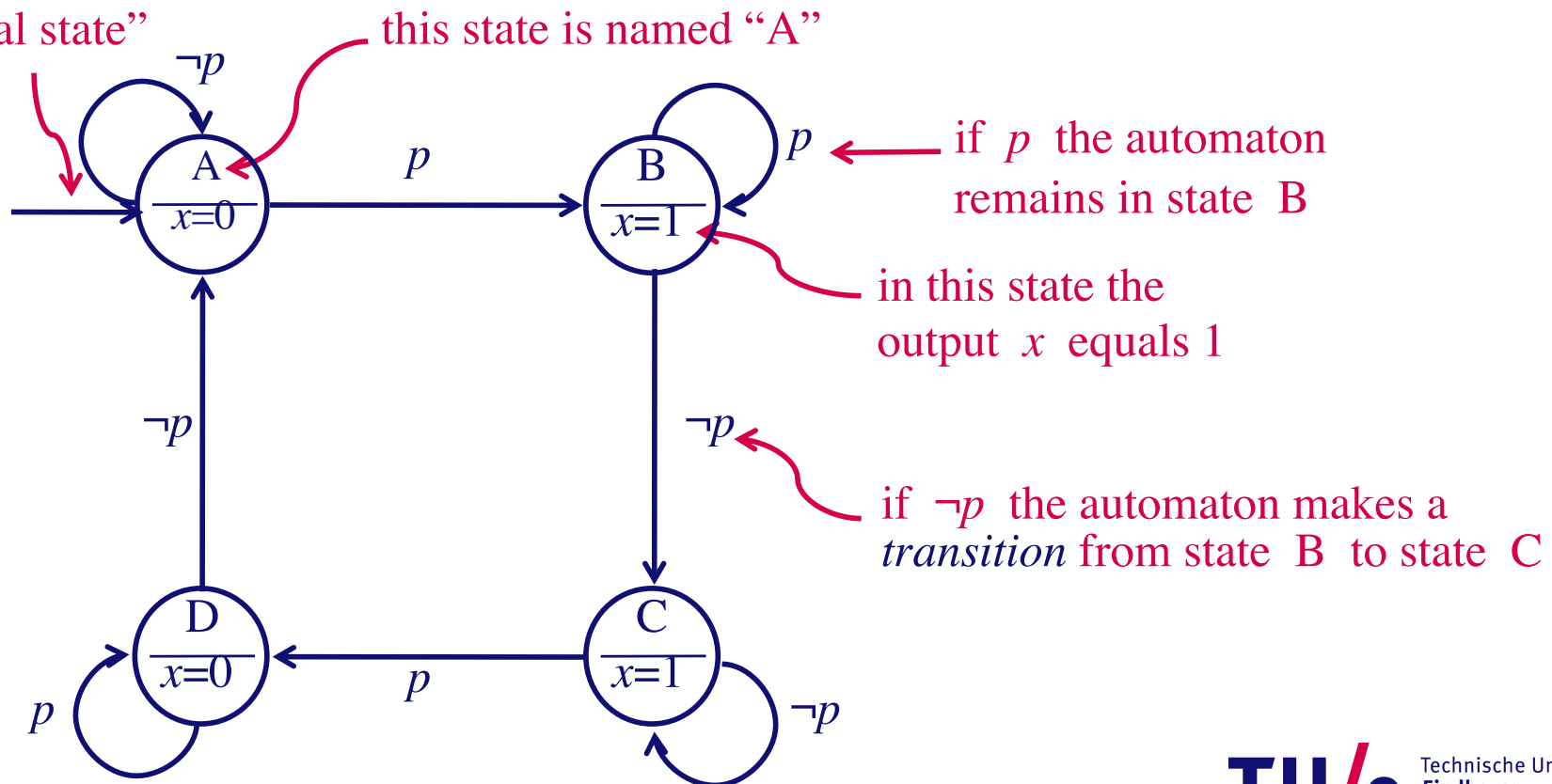

Finite Automata: Considerations

- ❑ *Different* states are needed whenever *different* behaviour is required for the *same* input values.
- ❑ States may be *named* arbitrarily: letters, numbers, ... ; a binary representation is chosen later. The *starting state*, or: *initial state*, must be clearly indicated.
- ❑ *Transitions* between states are labelled with Boolean expressions, called *guards*: a transition from one state to a next happens only if the guard of that transition is **true**.
- ❑ *Moore Machine*: the outputs depend on the state only, not (directly) on the inputs (we mainly use Moore Machines).
- ❑ *Mealy Machine*: the outputs may depend on the state and on the inputs.


Example: the On-Off Switch (1)

Specification

If the push button is pressed, the light goes “on”, and stays “on”; if the same button is pressed again the light goes “off”, and stays “off”, and so on indefinitely.

Variables

 $\neg p$: the push button is “open”
 p : the push button is “closed”
 $\neg x$: the light is “off”
 x : the light is “on”



Convention

- If, in any state, no outgoing transition is *enabled* –has a true guard–, then the automaton remains in its current state;
- Transitions from a state to itself often are not drawn: yields a cleaner drawing.

Example: the On-Off Switch (2)

Output table and State-transition table


From the state-transition diagram we derive an *output table* and an (abstract) *state-transition table*, in terms of the (abstract) names assigned to the states.

output table

| state | x |
|-------|-----|
| A | 0 |
| B | 1 |
| C | 1 |
| D | 0 |

state-transition table

| state | p | state _{new} |
|-------|-----|----------------------|
| A | 0 | A |
| A | 1 | B |
| B | 1 | B |
| B | 0 | C |
| C | 0 | C |
| C | 1 | D |
| D | 1 | D |
| D | 0 | A |

 

Example: the On-Off Switch (3)

State assignment

Several different state assignments are possible; binary representation of 4 states requires *at least* 2 bits, for example:

just counting

| state | s | t |
|-------|-----|-----|
| A | 0 | 0 |
| B | 0 | 1 |
| C | 1 | 0 |
| D | 1 | 1 |

Gray code

| state | s | t |
|-------|-----|-----|
| A | 0 | 0 |
| B | 1 | 0 |
| C | 1 | 1 |
| D | 0 | 1 |

one-hot encoding

| state | s_A | s_B | s_C | s_D |
|-------|-------|-------|-------|-------|
| A | 1 | 0 | 0 | 0 |
| B | 0 | 1 | 0 | 0 |
| C | 0 | 0 | 1 | 0 |
| D | 0 | 0 | 0 | 1 |

Gray code: because the states A, B, C, D are passed *cyclically*, in a Gray encoding only a *single state variable* changes in each transition.

On-Off Switch example: the Gray encoding is very attractive because now:

$s=1 \Leftrightarrow x=1$, so the output x just equals state variable s .

One-hot encoding: In every state, *exactly one* state variable has value 1; although this requires more variables, hence: more D-flip-flops, this may yield simpler combinatorial circuits.

Example: the On-Off Switch (4)

Boolean Functions

We choose the Gray encoding for the states, because this makes the function for the output simple. From the (abstract) state-transition table we derive a (concrete) state-transition table:

| output | | | new states | | | new states | | | | |
|--------|-----|-----|------------|-----|----------------------|------------|-----|-----|------------------|------------------|
| s | t | x | state | p | state _{new} | s | t | p | s_{new} | t_{new} |
| 0 | 0 | 0 | A | 0 | A | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | A | 1 | B | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | B | 1 | B | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | B | 0 | C | 1 | 0 | 0 | 1 | 1 |
| | | | C | 0 | C | 1 | 1 | 0 | 1 | 1 |
| | | | C | 1 | D | 1 | 1 | 1 | 0 | 1 |
| | | | D | 1 | D | 0 | 1 | 1 | 0 | 1 |
| | | | D | 0 | A | 0 | 1 | 0 | 0 | 0 |

output function: $x = s$

Example: the On-Off Switch (5)

Karnaugh-map for s_{new}

| | | | | | | |
|-----|---|-----|---|---|---|---|
| | | s | 0 | 1 | 1 | 0 |
| | | t | 0 | 0 | 1 | 1 |
| p | 0 | | 0 | 1 | 1 | 0 |
| | 1 | | 1 | 1 | 0 | 0 |

just a 2-input MUX:

$$s_{\text{new}} = p \wedge \neg t \vee \neg p \wedge s$$

Karnaugh-map for t_{new}

| | | | | | | |
|-----|---|-----|---|---|---|---|
| | | s | 0 | 1 | 1 | 0 |
| | | t | 0 | 0 | 1 | 1 |
| p | 0 | | 0 | 1 | 1 | 0 |
| | 1 | | 0 | 0 | 1 | 1 |

another 2-input MUX:

$$t_{\text{new}} = \neg p \wedge s \vee p \wedge t$$

Observe risk for glitches!


Example: the On-Off Switch (6)

Asynchronous sequential circuit

Just two 2-input multiplexers with feedback:

$$s_{\text{new}} = p \wedge \neg t \vee \neg p \wedge s$$
 
$$t_{\text{new}} = \neg p \wedge s \vee p \wedge t$$



Advantages


- Very fast responses to input changes
- Very compact circuits
- No clock needed
- Low power consumption

Disadvantages

- Requires *extremely careful* design:
- Very sensitive to glitches.
- Particularly glitch sensitive if several state variables change simultaneously.
(Hence the Gray code!)

Example: the On-Off Switch


State-transition diagram

 

 Example: the On-Off Switch (7)

Synchronous sequential circuit: driven by a periodic “clock”

The same circuit with feedback, but via D-Flip-Flops:



$$s_{\text{new}} = p \wedge \neg t \vee \neg p \wedge s$$

$$t_{\text{new}} = \neg p \wedge s \vee p \wedge t$$

Example: the On-Off Switch (8)

Synchronous sequential circuit:

The same circuit with feedback, but via D-Flip-Flops.

Properties:

- response speed to input changes increases with the clock frequency:
the faster the better.
- **but:** the maximal clock frequency f_{\max} is limited by: $f_{\max} \leq 1/T$, where
(*)..... $t_{\text{pdc}} + t_{\text{pdf}} + t_{\text{su}} = T$; here:
 t_{pdc} = “propagation delay of the combinatorial circuit”,
 t_{pdf} = “propagation delay of the D-Flip-Flop”,
 t_{su} = “setup time of the D-Flip-Flop”.
- if requirement (*) is met: glitches in the combinatorial circuit are
harmless: they will have died out before the next clock transition.


Example: the On-Off Switch with a double clock

Synchronous sequential circuit: driven by a double “clock”

The same circuit with feedback, but via four D-Flip-Flops:

$$s_{\text{new}} = p \wedge \neg t \vee \neg p \wedge s$$
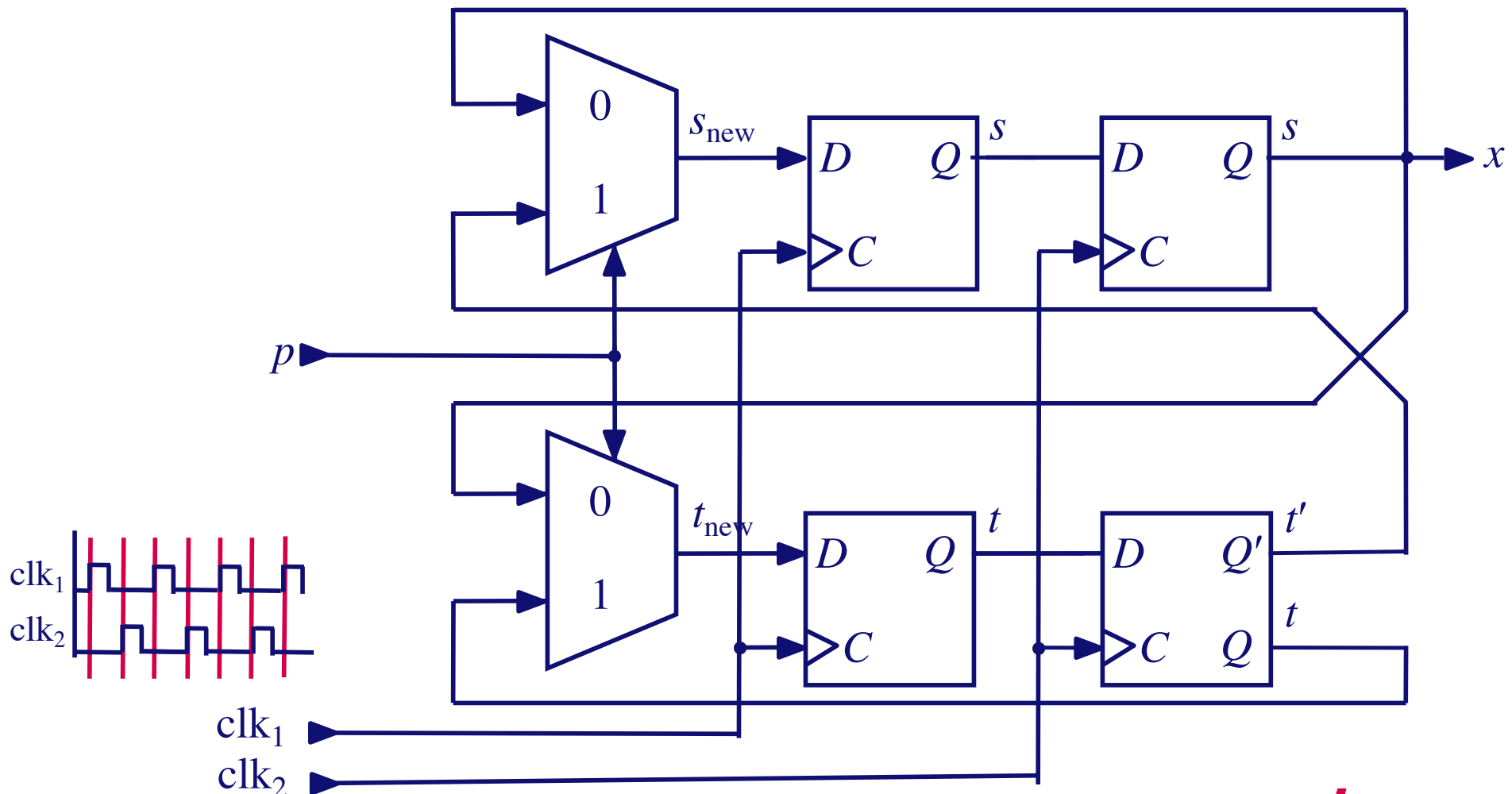
$$t_{\text{new}} = \neg p \wedge s \vee p \wedge t$$



Summary

What did you learn:

- Registers are made from multiple flip-flops.
- Using an input enable signal registers can be instructed to read.
- Using three state outputs and an output enable results from multiple register can be selected.
- Specify machines with memory as state machines.
- Implement state machines using flip-flops and combinatorial circuit.
- Mealy machine transfer their input directly to the output. This is faster than Moore machines, and generally leads to a smaller number of states.