

2IC30: Computer Systems

Flip-flops and registers.

Jan Friso Groote




TU / **e**

Technische Universiteit
Eindhoven
University of Technology

Where innovation starts


Binary addition of n-bit numbers

multi-bit adder
(ripple-carry)

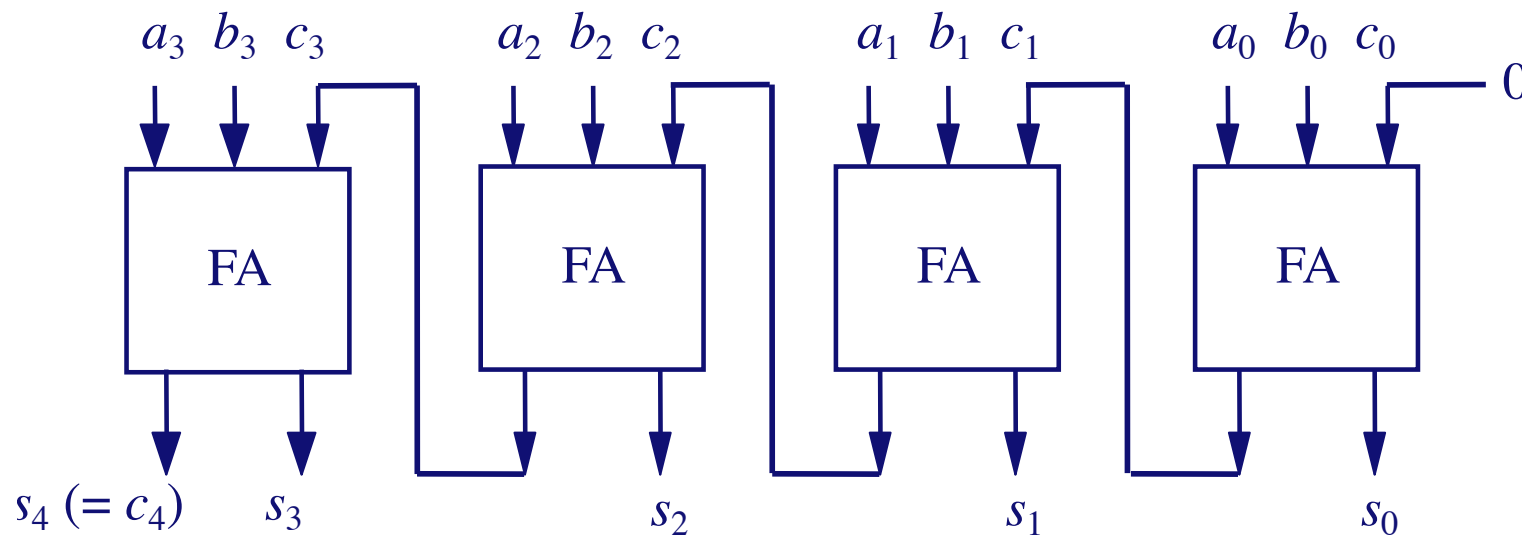

Adding a n-bit number requires $2n$ gate delays.
For 64-bit addition: $128+1$ gate delays.....



Solution: carry look ahead adder.

 


Multiplication.

$$\begin{array}{r}
 101 \\
 011 \times \\
 \hline
 101 \\
 101 \\
 000 + \\
 \hline
 01111
 \end{array}$$

	a_3	a_2	a_1	a_0				
	b_3	b_2	b_1	b_0				
	<hr/>							
	$a_3 \wedge b_0$	$a_2 \wedge b_0$	$a_1 \wedge b_0$	$a_0 \wedge b_0$				
	<hr/>							
	$a_3 \wedge b_1$	$a_2 \wedge b_1$	$a_1 \wedge b_1$	$a_0 \wedge b_1$	+			
	r_{51}	r_{41}	r_{31}	r_{21}	r_{11}	r_{01}		
	<hr/>							
	$a_3 \wedge b_2$	$a_2 \wedge b_2$	$a_1 \wedge b_2$	$a_0 \wedge b_2$	+			
	r_{62}	r_{52}	r_{42}	r_{32}	r_{22}	r_{12}	r_{02}	
	<hr/>							
	$a_3 \wedge b_3$	$a_2 \wedge b_3$	$a_1 \wedge b_3$	$a_0 \wedge b_3$	+			
	r_{73}	r_{63}	r_{53}	r_{43}	r_{33}	r_{23}	r_{13}	r_{03}

 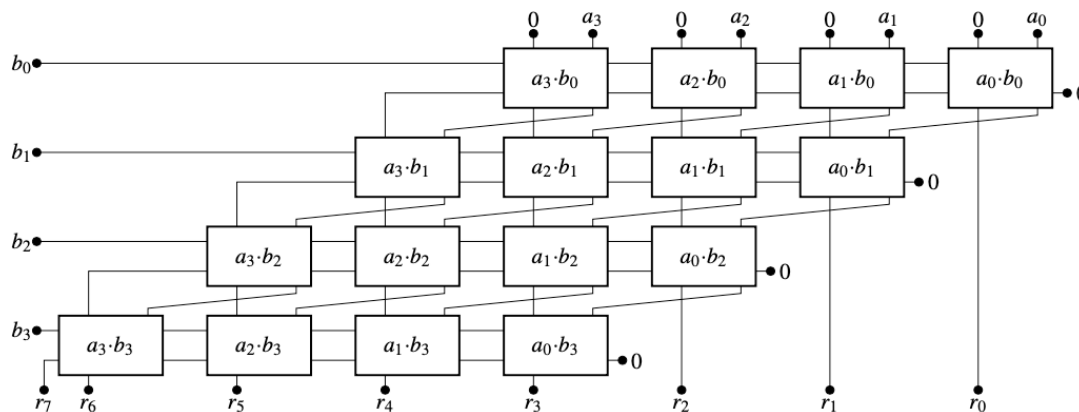

The adder is part of the ALU

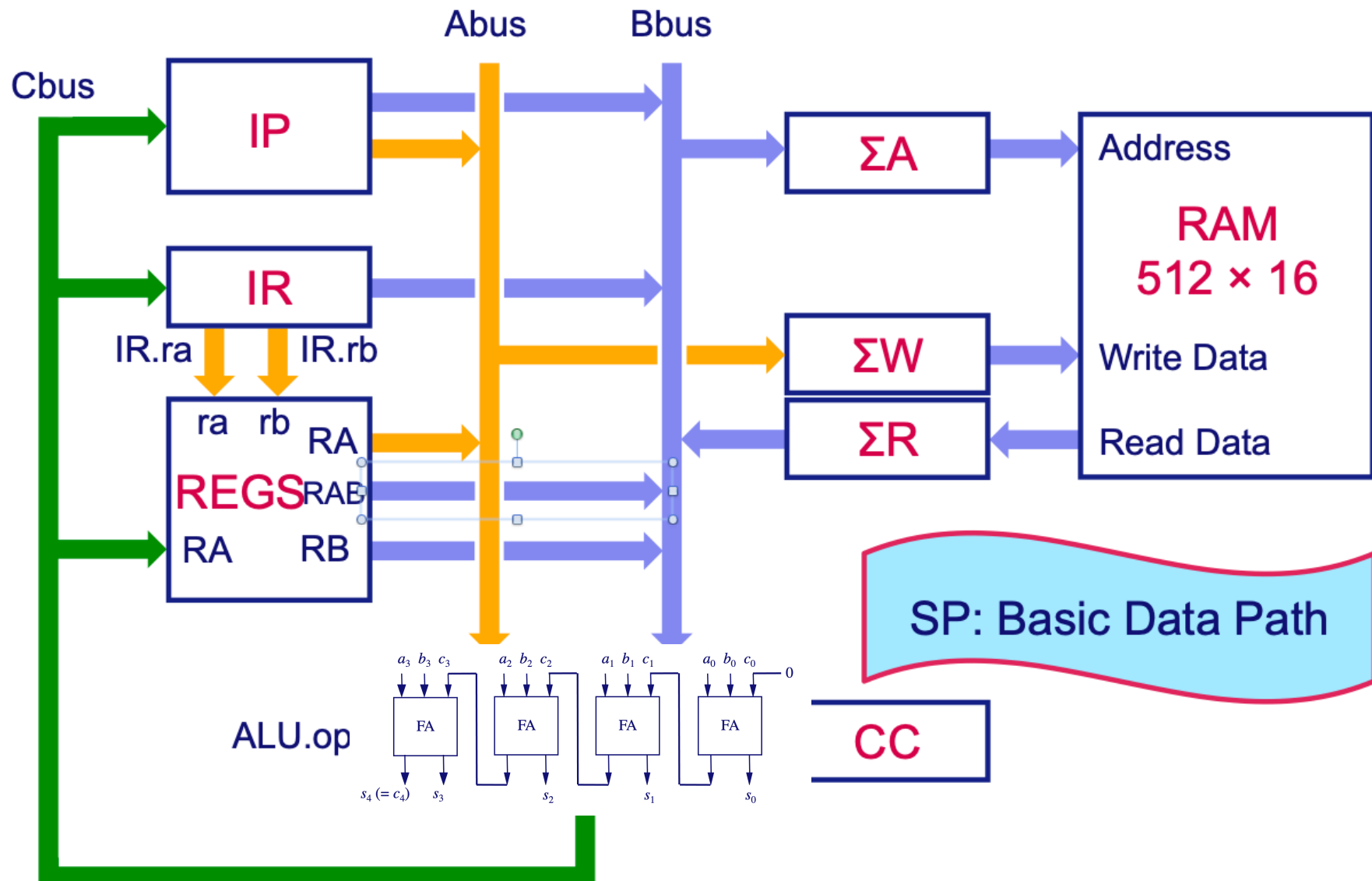



Other number systems: Gray codes

b ₃	b ₂	b ₁	b ₀	decimal	hexadecimal	octal
0	0	0	0	0	0	00
0	0	0	1	1	1	01
0	0	1	0	2	2	02
0	0	1	1	3	3	03
0	1	0	0	4	4	04
0	1	0	1	5	5	05
0	1	1	0	6	6	06
0	1	1	1	7	7	07
1	0	0	0	8	8	10
1	0	0	1	9	9	11
1	0	1	0	10	A	12
1	0	1	1	11	B	13
1	1	0	0	12	C	14
1	1	0	1	13	D	15
1	1	1	0	14	E	16
1	1	1	1	15	F	17



Other number systems: Gray codes

b_3	b_2	b_1	b_0	decimal	hexadecimal	octal
0	0	0	0	0	0	00
0	0	0	1	1	1	01
0	0	1	1	2	2	02
0	0	1	0	3	3	03
0	1	1	0	4	4	04
0	1	1	1	5	5	05
0	1	0	1	6	6	06
0	1	0	0	7	7	07
1	1	0	0	8	8	10
1	1	0	1	9	9	11
1	1	1	1	10	A	12
1	1	1	0	11	B	13
1	0	1	0	12	C	14
1	0	1	1	13	D	15
1	0	0	1	14	E	16
1	0	0	0	15	F	17

  

Error detecting codes: add a parity bit

b ₃	b ₂	b ₁	b ₀	parity bit
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

If the parity bit is incorrect
data, the data is corrupted.

More expensive memory has
parity bits built in.

IBM is contemplating adding
parities to all aspects of
safety critical processors

Error correcting codes: Hamming codes.

By adding a few more bits to each word, some bits can even be corrected.

In the table below it is indicated how much extra information is required to correct one bit.

Bit position		1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
Encoded data bits		p1	p2	d1	p4	d2	d3	d4	p8	d5	d6	d7	d8	d9	d10	d11	p16	d12	d13	d14	d15
Parity bit coverage	p1	X		X		X		X		X		X		X		X		X		X	
	p2		X	X			X	X			X	X			X	X			X	X	
	p4				X	X	X	X					X	X	X	X					X
	p8								X	X	X	X	X	X	X	X					
	p16																X	X	X	X	X

source: Wikipedia.

Other codes.

Self delimiting codes: first indicate how long a number is.

1 0 1 0 1 1 - 1 0 0 1 0 1 1 75



Red bits are end of header indicators. Other initial bits indicate length of data to follow. In this case the length is 7 bits, with a header of 6 bits.

ASCII code for characters

Unicode: 64 bit representation for characters.


Huffman codes: assign shorter bit sequences to more often occurring objects.

Hex	Dec	Char	Hex	Dec	Char	Hex	Dec	Char	Hex	Dec	Char
0x00	0	NULL null	0x20	32	Space	0x40	64	@	0x60	96	`
0x01	1	SOH Start of heading	0x21	33	!	0x41	65	A	0x61	97	a
0x02	2	STX Start of text	0x22	34	"	0x42	66	B	0x62	98	b
0x03	3	ETX End of text	0x23	35	#	0x43	67	C	0x63	99	c
0x04	4	EOT End of transmission	0x24	36	\$	0x44	68	D	0x64	100	d
0x05	5	ENQ Enquiry	0x25	37	%	0x45	69	E	0x65	101	e
0x06	6	ACK Acknowledge	0x26	38	&	0x46	70	F	0x66	102	f
0x07	7	BELL Bell	0x27	39	'	0x47	71	G	0x67	103	g
0x08	8	BS Backspace	0x28	40	(0x48	72	H	0x68	104	h
0x09	9	TAB Horizontal tab	0x29	41)	0x49	73	I	0x69	105	i
0x0A	10	LF New line	0x2A	42	*	0x4A	74	J	0x6A	106	j
0x0B	11	VT Vertical tab	0x2B	43	+	0x4B	75	K	0x6B	107	k
0x0C	12	FF Form Feed	0x2C	44	,	0x4C	76	L	0x6C	108	l
0x0D	13	CR Carriage return	0x2D	45	-	0x4D	77	M	0x6D	109	m
0x0E	14	SO Shift out	0x2E	46	.	0x4E	78	N	0x6E	110	n
0x0F	15	SI Shift in	0x2F	47	/	0x4F	79	O	0x6F	111	o
0x10	16	DLE Data link escape	0x30	48	0	0x50	80	P	0x70	112	p
0x11	17	DC1 Device control 1	0x31	49	1	0x51	81	Q	0x71	113	q
0x12	18	DC2 Device control 2	0x32	50	2	0x52	82	R	0x72	114	r
0x13	19	DC3 Device control 3	0x33	51	3	0x53	83	S	0x73	115	s
0x14	20	DC4 Device control 4	0x34	52	4	0x54	84	T	0x74	116	t
0x15	21	NAK Negative ack	0x35	53	5	0x55	85	U	0x75	117	u
0x16	22	SYN Synchronous idle	0x36	54	6	0x56	86	V	0x76	118	v
0x17	23	ETB End transmission block	0x37	55	7	0x57	87	W	0x77	119	w
0x18	24	CAN Cancel	0x38	56	8	0x58	88	X	0x78	120	x
0x19	25	EM End of medium	0x39	57	9	0x59	89	Y	0x79	121	y
0x1A	26	SUB Substitute	0x3A	58	:	0x5A	90	Z	0x7A	122	z
0x1B	27	FSC Escape	0x3B	59	;	0x5B	91	[0x7B	123	{
0x1C	28	FS File separator	0x3C	60	<	0x5C	92	\	0x7C	124	
0x1D	29	GS Group separator	0x3D	61	=	0x5D	93]	0x7D	125	}
0x1E	30	RS Record separator	0x3E	62	>	0x5E	94	^	0x7E	126	~
0x1F	31	US Unit separator	0x3F	63	?	0x5F	95	_	0x7F	127	DEL

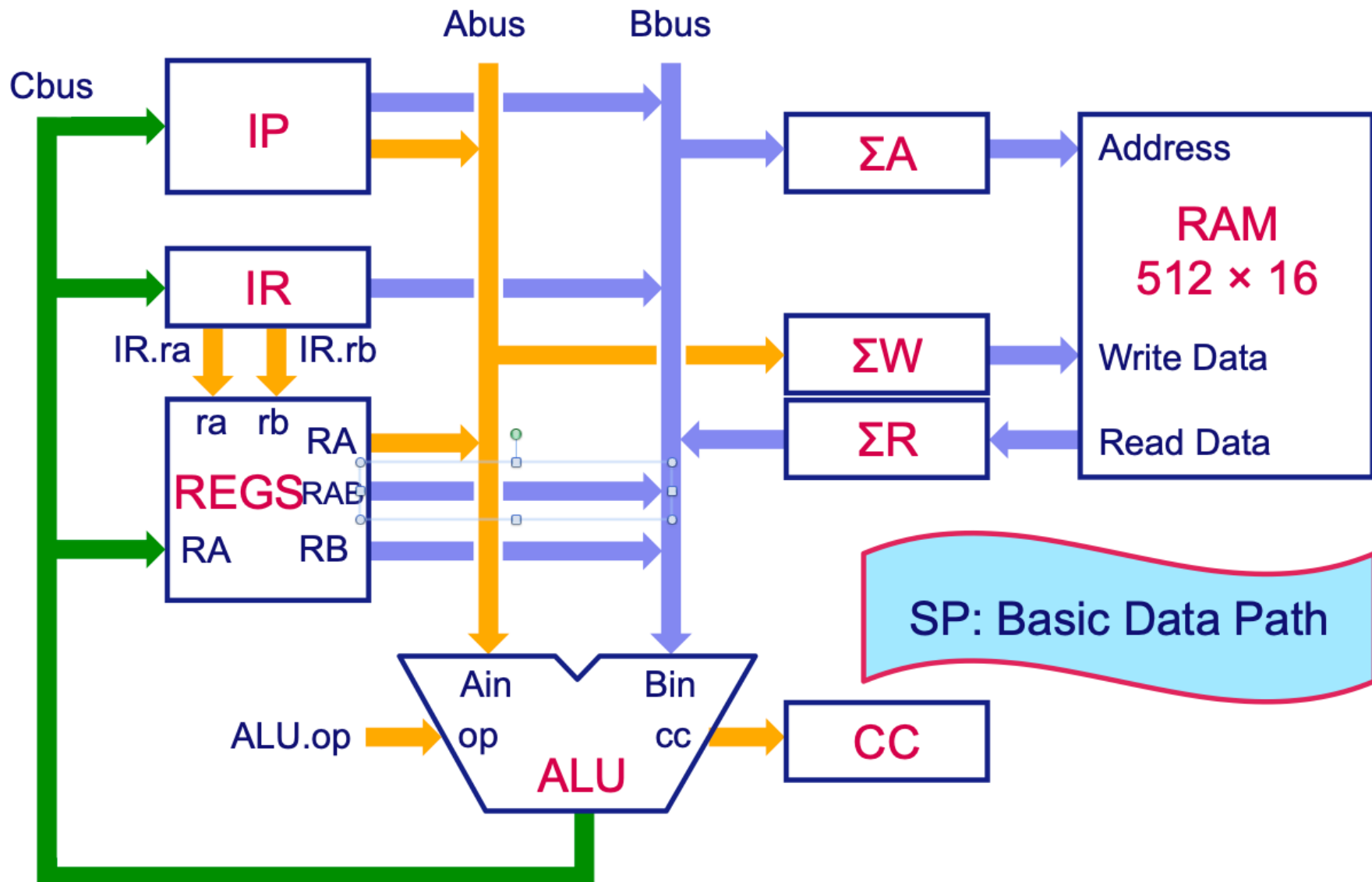Questions?



A microprocessor stores data in registers




Remembering the past: Circuits with States

□ Circuits with feedback:

- Set-Reset Latch/Flip-Flop
- Level triggered Flip-Flop: D-Latch
- Edge triggered Flip-Flop: D-Flip-Flop

A simple memory cell

 

simple memory cell

S	y	Q	
0	0	0	\Leftarrow <i>stable</i> : $y = 0$
0	1	1	\Leftarrow <i>stable</i> : $y = 1$
1	0	1	\Leftarrow <i>unstable</i> : $y := 1$
1	1	1	\Leftarrow <i>stable</i> : $y = 1$


Idea:

- ❑ if (initially) $Q = 0$ and $S = 0$ then Q “remains” 0
- ❑ if $S = 1$ then Q “becomes” 1
- ❑ if $Q = 1$ then Q “remains” 1 (forever...)
- ❑ example of *positive feedback*: no signal inversions
- ❑ so: $Q = 1$ “remembers” that, once upon a time in the past, S has been 1 for a while

Problem:

- ❑ once $Q = 1$ it will stay 1: how to *reset* Q back to 0?

Duality: another simple memory cell

 

simple memory cell

R	z	Q	
0	0	0	\Leftarrow <i>stable</i> : $z = 0$
0	1	0	\Leftarrow <i>unstable</i> : $z := 0$
1	0	0	\Leftarrow <i>stable</i> : $z = 0$
1	1	1	\Leftarrow <i>stable</i> : $z = 1$


Idea:

- ❑ if (initially) $Q = 1$ and $R = 1$ then Q “remains” 1
- ❑ if $R = 0$ then Q “becomes” 0
- ❑ if $Q = 0$ then Q “remains” 0 (forever...)
- ❑ example of *positive feedback*: no signal inversions
- ❑ so: $Q = 0$ “remembers” that, once upon a time in the past, R has been 0 for a while

 Problem:


- ❑ once $Q = 0$ it will stay 0 : how to *reset* Q back to 1 ?

The Set-Reset Latch (S-R Latch/Flip Flop)



S-R Latch with NORs


S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	0	0

 

S-R Latch with NANDs

S	R	Q	Q'
0	0	1	1
0	1	0	1
1	0	1	0
1	1	Q	Q'

Problems with the S-R Latch


 


S-R Latch with NANDs


S	R	Q	Q'
0	0	1	1
0	1	0	1
1	0	1	0
1	1	Q	Q'

- **Glitches:** Unintended temporary changes in S or R may cause unintended state changes in Q (and Q').
- **Metastability:** Unpredictable behaviour when S and R make the transition from 0,0 to 1,1 *simultaneously*.

Glitches: temporary signal deviations

  

Gated S-R Latch

 


- ❑ if $E = 0$ then Q and Q' are stable and not sensitive to (changes in) S and R ; glitches on S or R are harmless
- ❑ if $E \wedge S \wedge \neg R$ then $Q := 1$ and $Q' := 0$
- ❑ if $E \wedge \neg S \wedge R$ then $Q := 0$ and $Q' := 1$
- ❑ if $E \wedge S \wedge R$ then $Q := 1$ and $Q' := 1$: risk of *metastability*
- ❑ if $E \wedge \neg S \wedge \neg R$ then “no change in Q and Q' ”

Requirements:

- ❑ to prevent *metastability*, $S \neq R$ is needed whenever $E = 1$


Gated S-R Latch: Timing diagram

 

Disadvantage: Signals S and R may be equal and, hence, cause metastability problems.

Improvement: the gated D-Latch.

Gated D-Latch (or: Transparent Latch)

 


- ❑ Signals S and R are now *derived* from D , in such a way that always $S \neq R$.
- ❑ **If $E = 0$ then** Q and Q' are stable and insensitive to changes in D ; glitches on D are harmless.
- ❑ **If $E = 1$ then** $Q = D$ and $Q' = \neg D$: the outputs follow D .

Requirements:

- ❑ As long as $E = 1$ input D must be *stable*.


Gated D-Latch: Timing diagram

 


Disadvantage: When E remains 1 for a long time, D must remain stable for an equally long time.

Improvement: the Edge-Triggered D-Flip-Flop.



An Edge Detector, or: pulse shaper

 

 Exploiting the **delay** of a (slow) inverter, that is: putting a glitch to good use.



  Clocked D-Flip-Flop (or: Edge-Triggered FF)




edge-triggered D-flip-flop

- on $C \uparrow$ then $Q := D$ and $Q' := \neg D$: the outputs copy D on every *upgoing transition* on C .

Requirement:

- Input D must be *stable* only during a short interval around $C \uparrow$: the *setup-and-hold interval*.

Clocked D-Flip-Flop: Timing diagram

 


t_{su} (“setup time”): the *minimal* amount of time D must be stable *before* $C \uparrow$.

t_{dh} (“hold time”): the *minimal* amount of time D must be stable *after* $C \uparrow$.


t_{oh} (“output hold time”): the *minimal* amount of time *after* $C \uparrow$ during which Q and Q' will retain their *old* values.

t_{pd} (“propagation delay”): the *maximal* amount of time *after* $C \uparrow$ before Q and Q' have obtained their *new* values.


Clocked D-Flip-Flop: Timing properties

 

 
- t_{su} might be *negative*: why?
- *always*: $0 < t_{su} + t_{dh}$: why?
- *always*: $0 \leq t_{oh} \leq t_{pd}$: why?
- if $t_{dh} \leq t_{oh}$ D-Flip-Flops can be *cascaded* (and work correctly):




Clocked D-Flip-Flop: Timing properties

 

 
- t_{su} might be *negative*: why?
- *always*: $0 < t_{su} + t_{dh}$: why?
- *always*: $0 \leq t_{oh} \leq t_{pd}$: why?
- if $t_{dh} \leq t_{oh}$ D-Flip-Flops can be *cascaded* (and work correctly):



Latches versus Flip-Flops

 

edge-triggered D-flip-flop

 


transparent D-latch

circle would indicate
a falling edge
triggered circuit

edge triggered flip-flops copy values during a rising (or: falling) edge of the clock

transparent latches copy values while the enable signal is 1

timing diagram:

 


*behaviour is similar, except when
input D changes while clk = 1*

Questions?



2-input multiplexer (= data selector)

 


$$f = a_0 \wedge \neg s \vee a_1 \wedge s$$

$$f = \text{if } s \text{ then } a_1 \text{ else } a_0$$

multiplexer

s	a_0	a_1	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

2-input multiplexer

s	f
0	a_0
1	a_1

4-input multiplexer (= data selector)


4-input multiplexer
(abstract)

s	f
0	a_0
1	a_1
2	a_2
3	a_3


4-input multiplexer
(binary)

s_1	s_0	f
0	0	a_0
0	1	a_1
1	0	a_2
1	1	a_3


symbol

 

 4-input multiplexer: built from 2-input MUX-es



4-input multiplexer: two-level circuit

 

Multiplexers as Universal Function Blocks


4-valued function
(abstract)

s	$f(s)$
0	$f(0)$
1	$f(1)$
2	$f(2)$
3	$f(3)$

boolean function of 2
boolean variables


s_1	s_0	$f(s_1, s_0)$
0	0	$f(0,0)$
0	1	$f(0,1)$
1	0	$f(1,0)$
1	1	$f(1,1)$

MUX-implementation

 


A multiplexer to implement standard gates.

NAND gate

 

Exclusive OR gate

 

Questions?



Summary

What did you learn:

- Carry look ahead adder, multiplication, alternative codes.
- S/R-flip-flops, D-latches and D-flip-flops.
- Glitches and meta-stability.
- How to construct larger multiplexers from simple multiplexers.
- How to use multiplexers to construct more combinatorial gates and circuits.